Circuit Diagram -

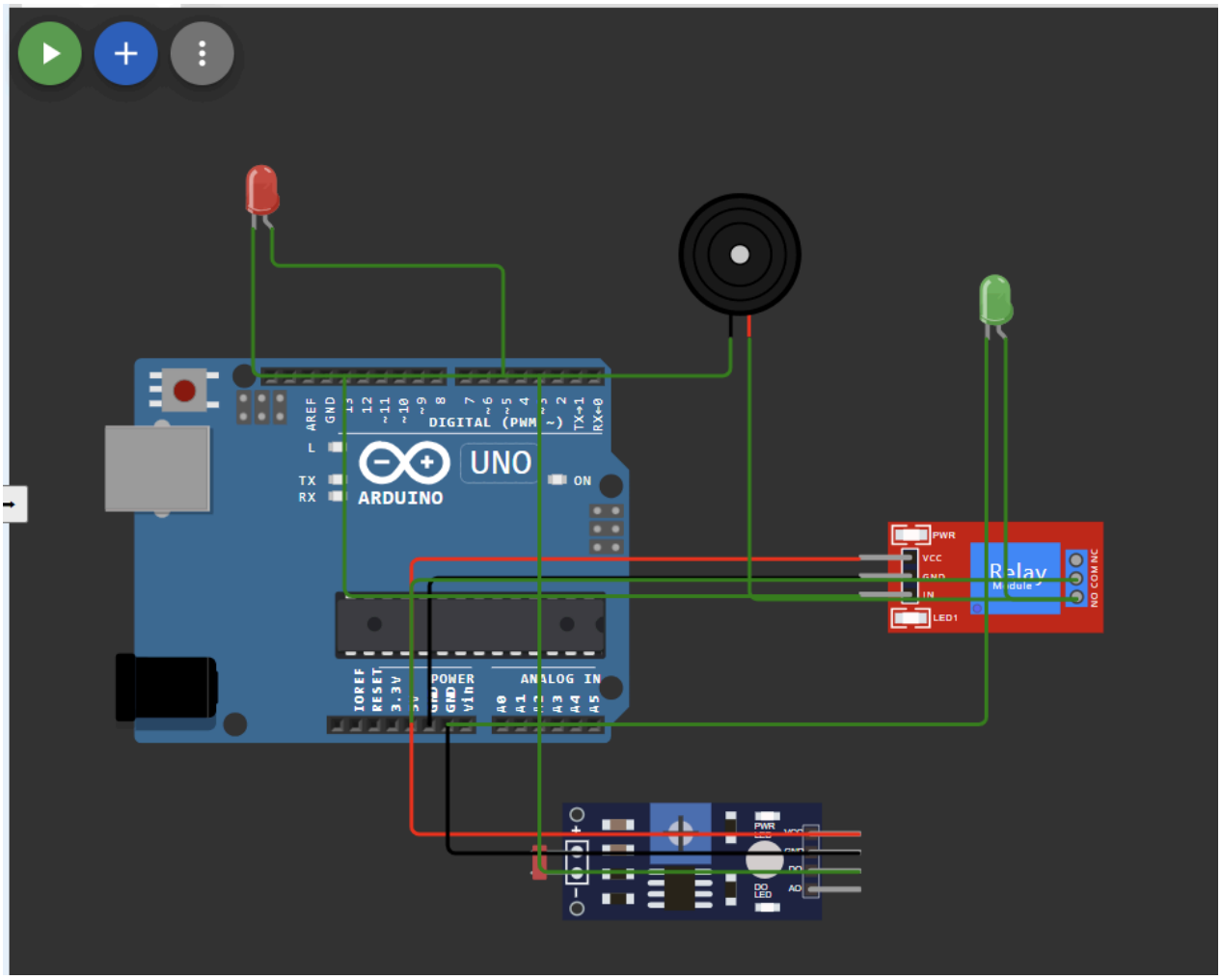

Result Screenshots -

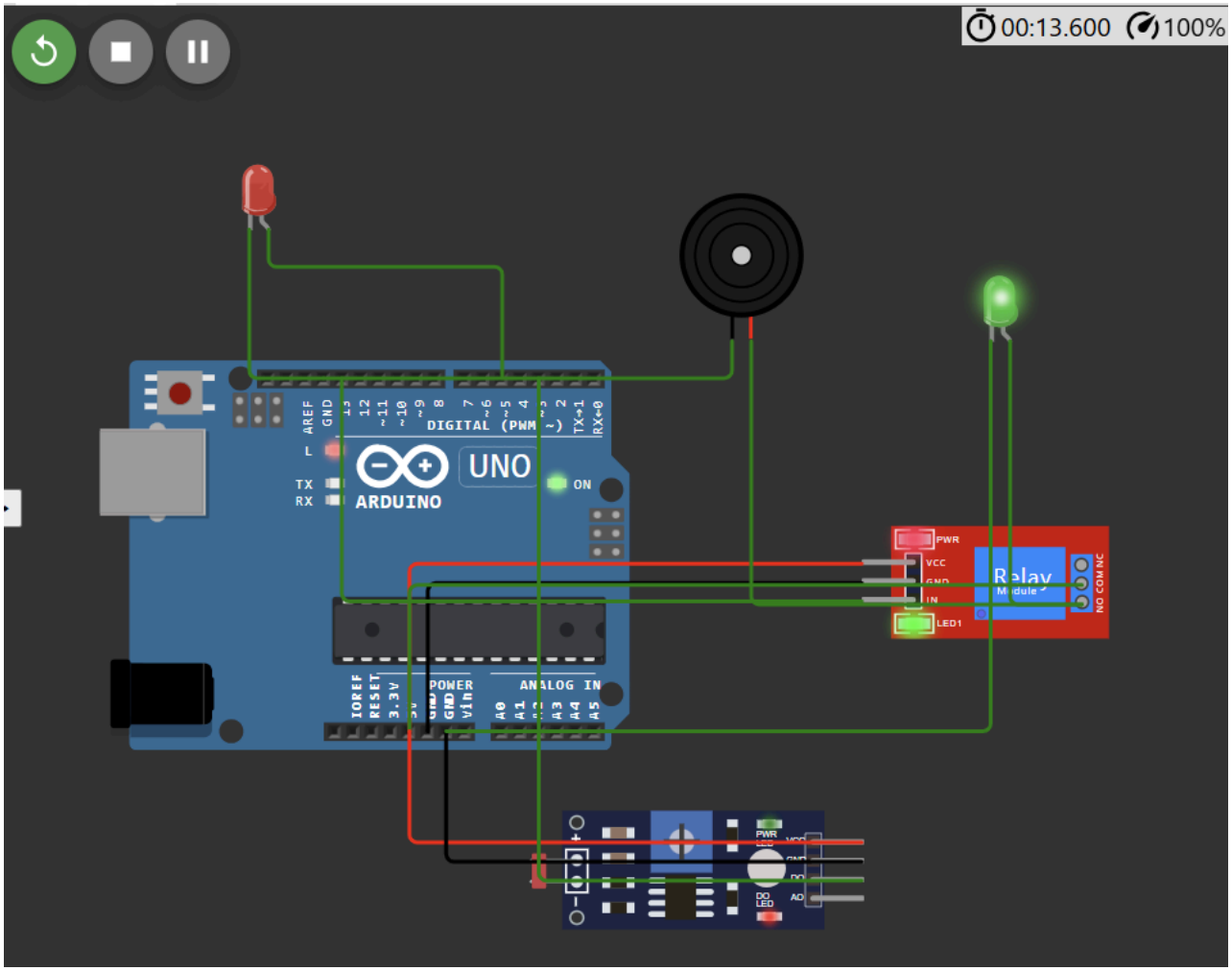
00:13.600
100%
UNO
ARDUINO
DIGITAL (PWM ~)
POWER
ANALOG IN
PWR
VCC
GND
IN
LED1
Relay
Module
NO COM NC